


Auctioneering Diodes: Pros and Cons

Norbert Doerry
Naval Sea Systems Command

Robert Ashton
Ashton Consulting LLC

2019 IEEE Electric Ship Technologies Symposium (ESTS 2019)
August 14-16, 2019
Arlington VA



Asymmetric Auctioneering Diodes

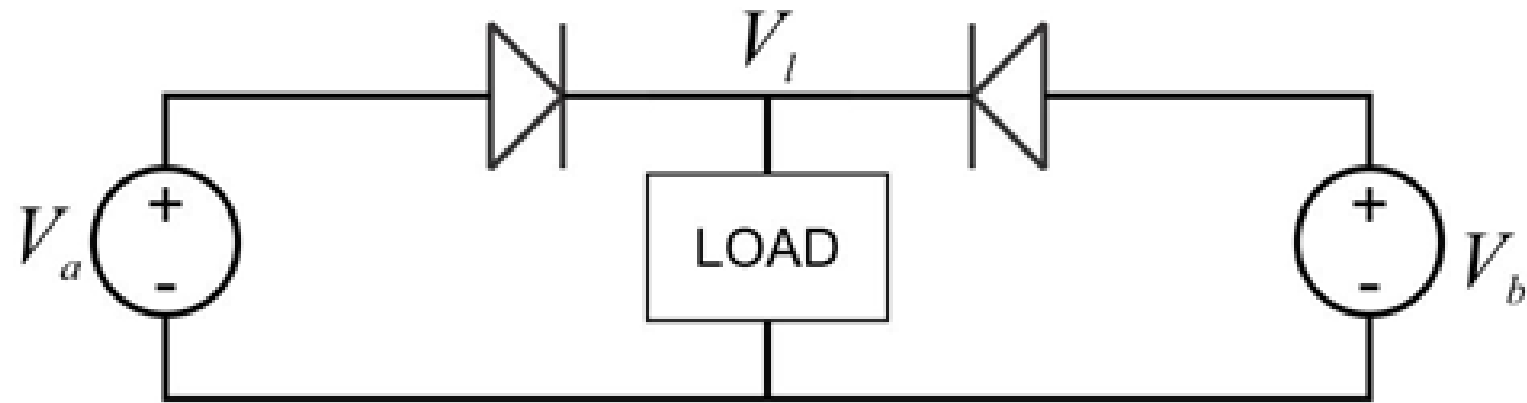

Uninterruptible power to load if either source faults


Asymmetric Auctioneering Diodes: Multiple Loads

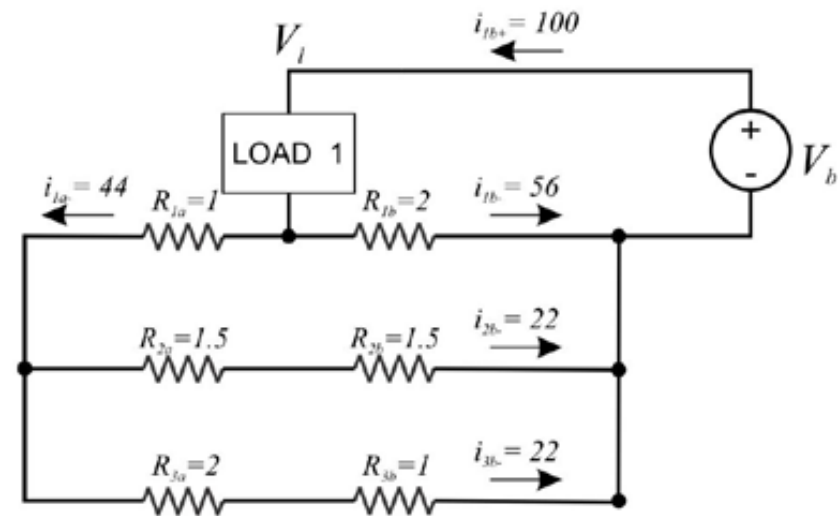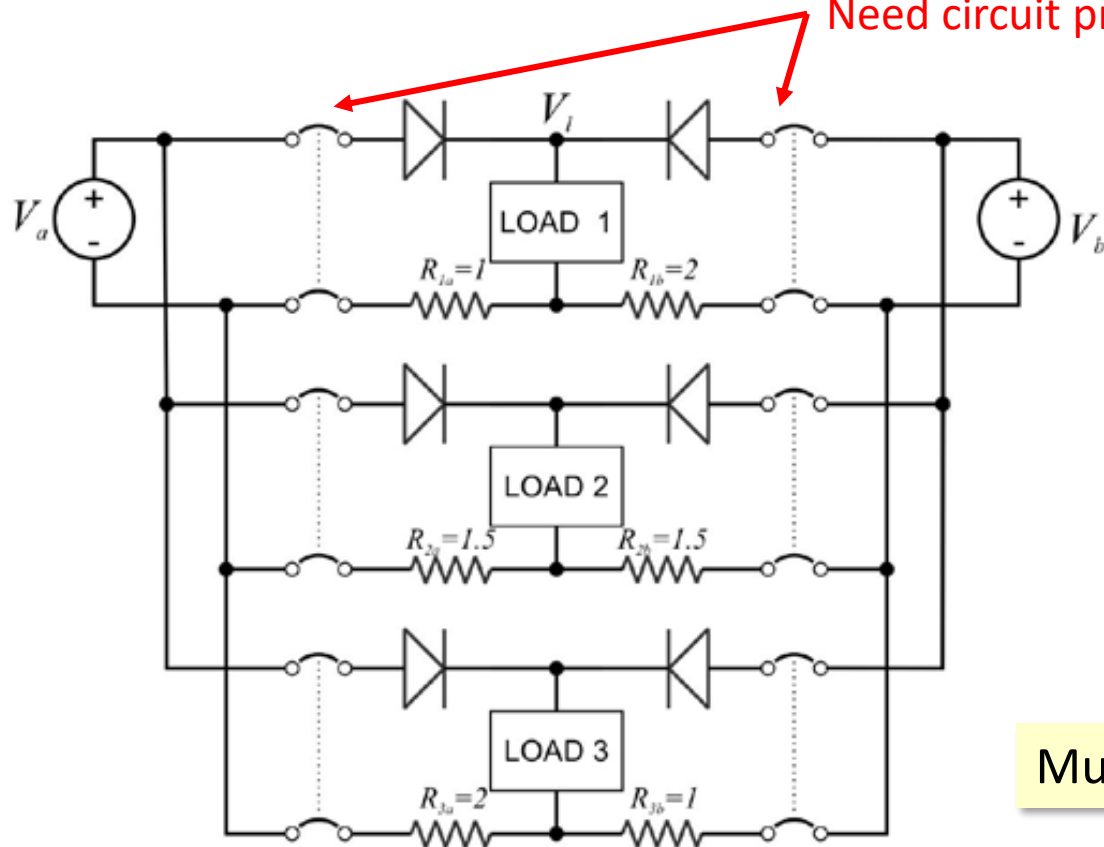Need circuit protection to avoid single point of failure



Multiple return paths result in common mode currents



Symmetric Auctioneering Diodes

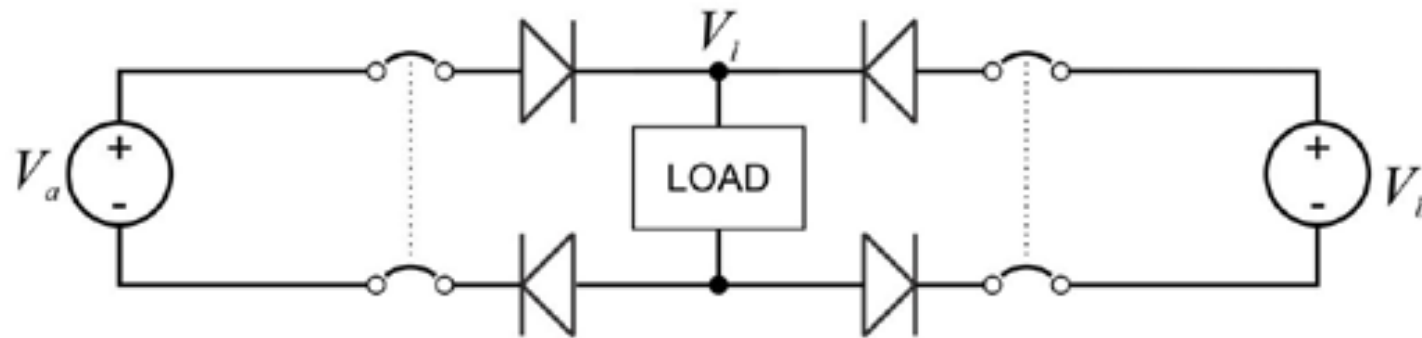



Eliminates multiple return paths and associated common mode currents

Symmetric Auctioneering Diodes: Double Ground Fault


Voltage doubles on double ground fault

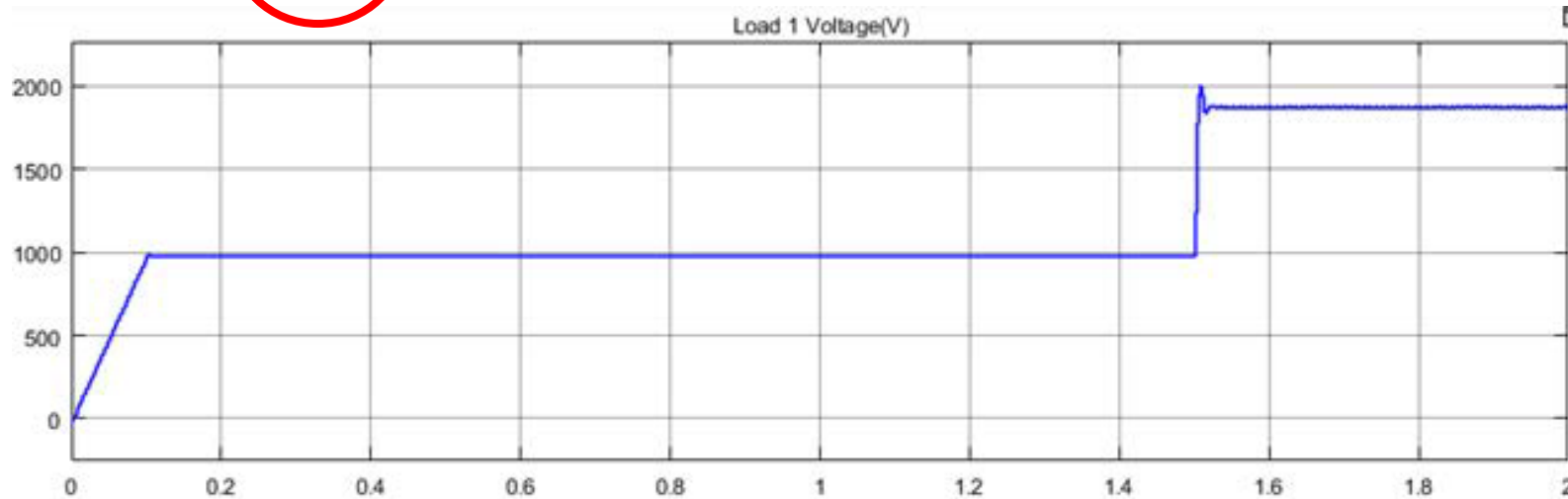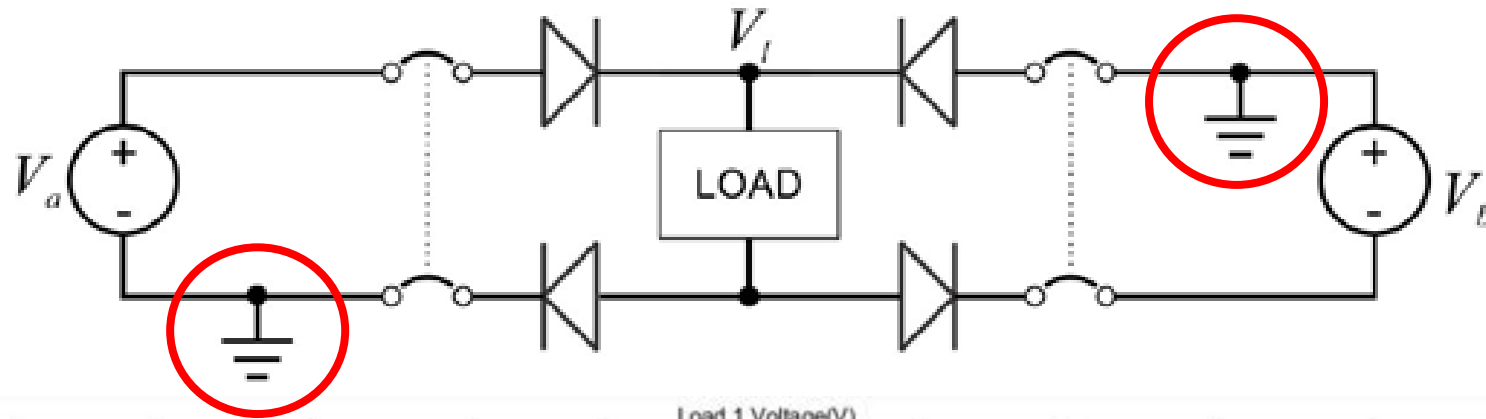

Diode Snubber

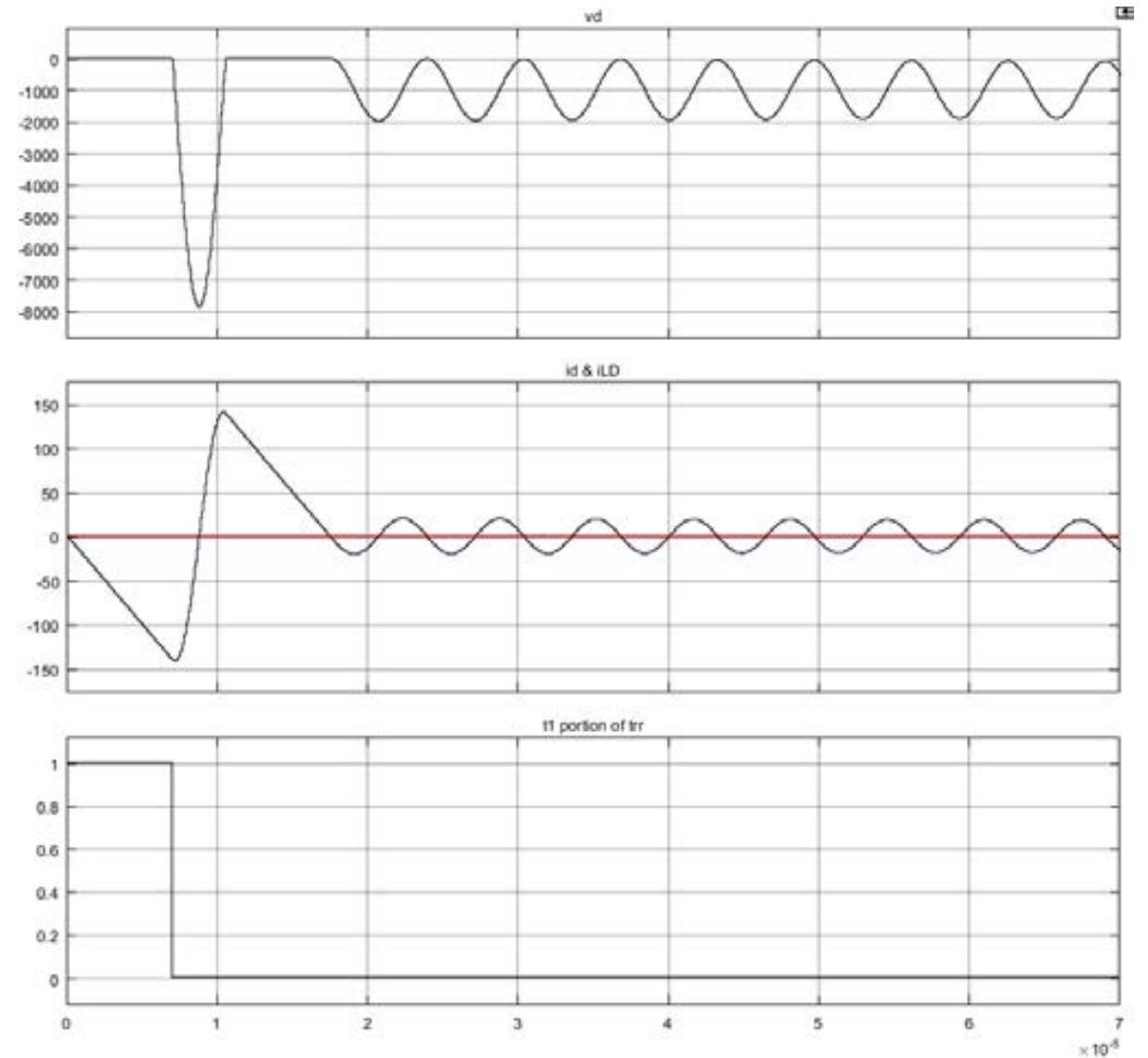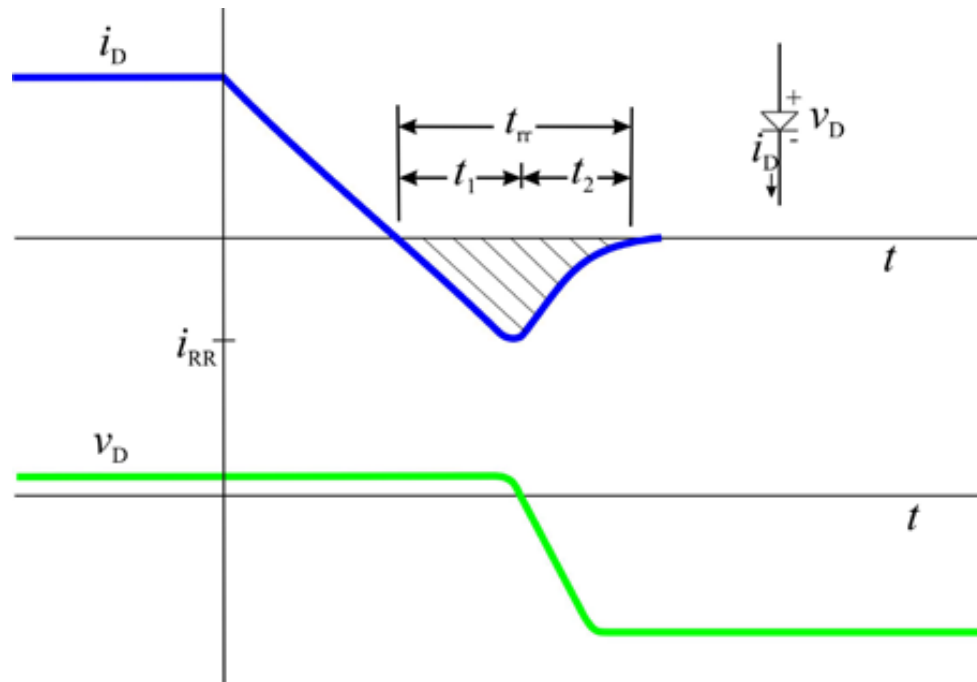

Diode Snubber

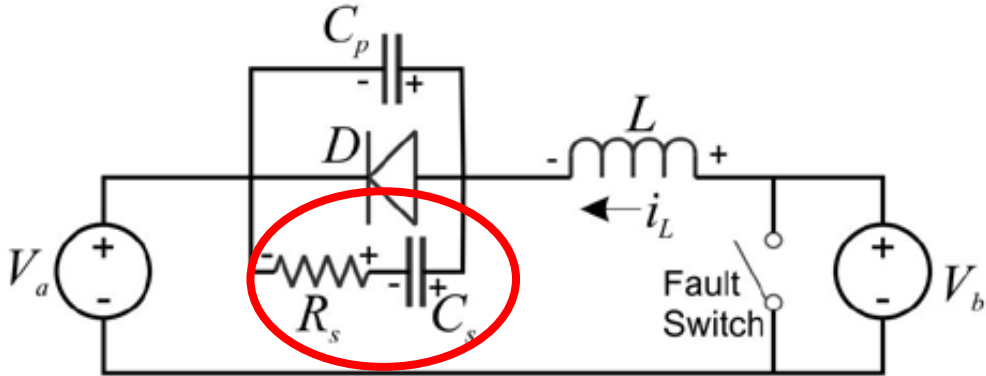

$$i_L(0) = -i_{RR} \quad V_{CS}(0) = 0 \quad (1)$$

$$-V_a = L \frac{di_L}{dt} + R_s i_L + V_{CS} \quad (2)$$

$$i_L = C_s \frac{dV_{CS}}{dt} \quad \text{or} \quad \frac{di_L}{dt} = C_s \frac{d^2V_{CS}}{dt^2} \quad (3)$$

Combining (2) and (3) results in (4)

$$-V_a = LC_s \frac{d^2V_{CS}}{dt^2} + R_s C_s \frac{dV_{CS}}{dt} + V_{CS} \quad (4)$$

Minimum capacitance (critically damped)

$$C_s = \frac{4L}{R_s^2}$$



Minimum capacitance (Avoid interaction with Cp)

$$C_s > 3C_p$$

Limit initial spike to a value diode can tolerate

$$R_s = \frac{V_a}{i_{RR}}$$

Diode Snubber

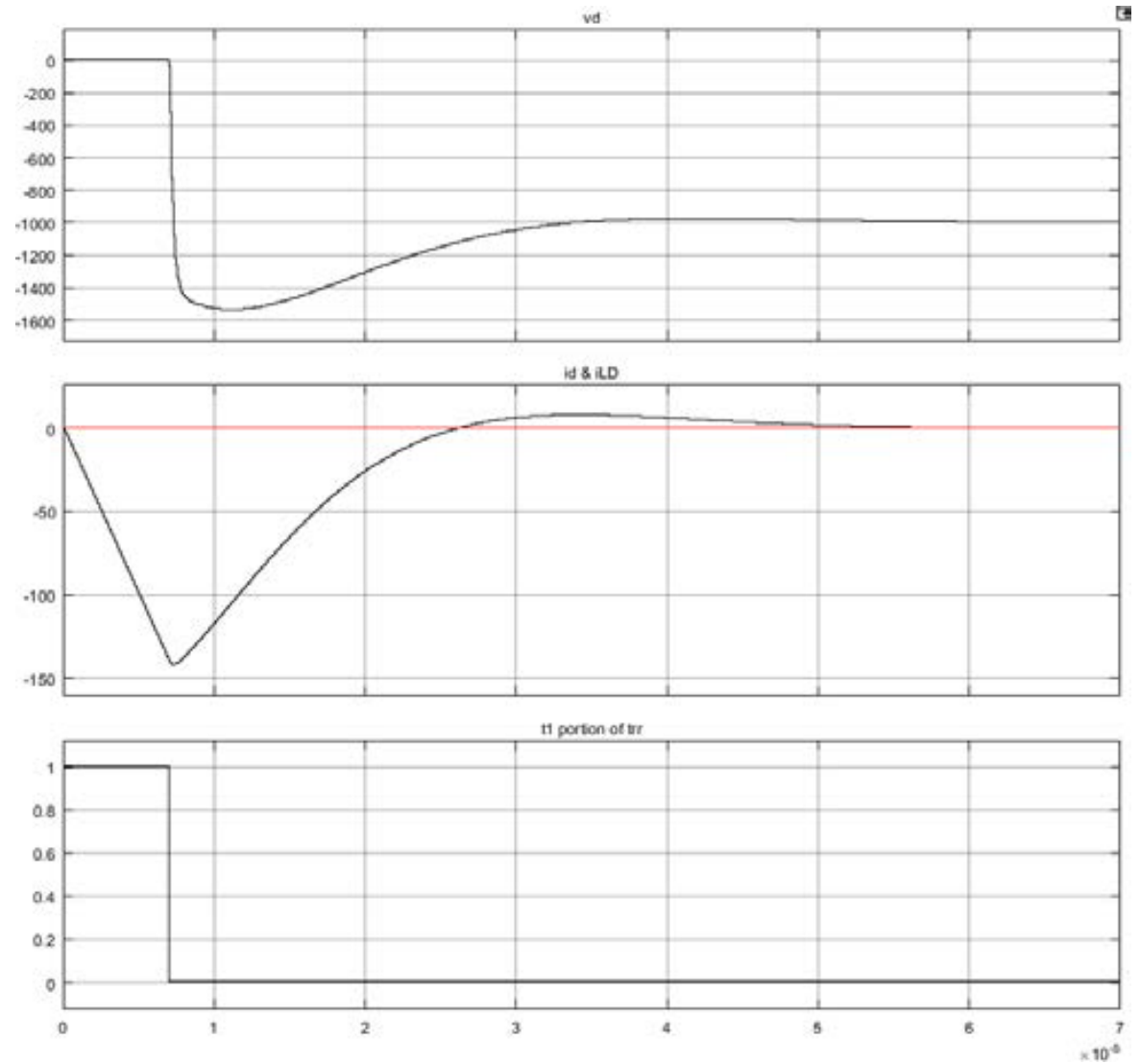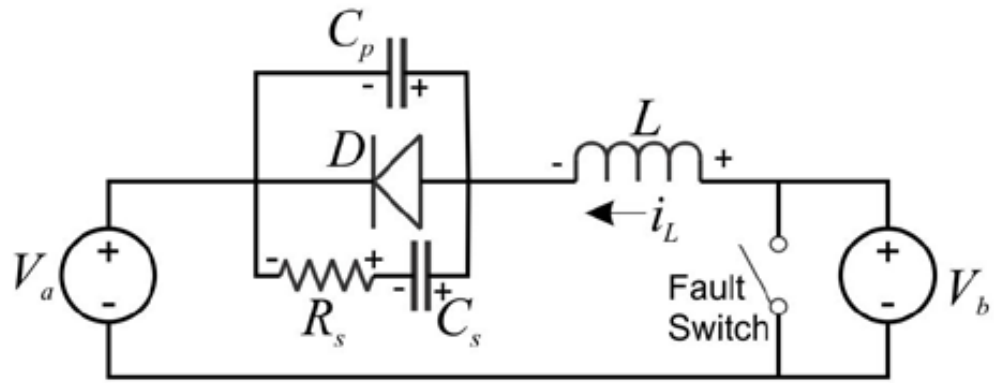

Summary

- Asymmetric Auctioneering Diodes
 - Great for single loads
 - Issues with multiple loads
 - Requires circuit protection
 - Common mode currents
- Symmetric Auctioneering Diodes
 - Eliminates common mode issue of Asymmetric configuration
 - Still requires circuit protection for multiple loads
 - Voltage doubling issue with double ground faults
- Diode Snubbers
 - May be required due to reverse recovery current of diodes