Solidly Grounded Shipboard Systems

IEEE 45.1 Quarterly Meeting Norbert Doerry June 14, 2024 © 2024 Norbert Doerry

Solidly Grounded Shipboard Systems

- IEEE Std 45.1-2023 Section 25.2 states
 - "Secondary buses powering non-critical loads should be solidly grounded"
- Rationale
 - Promote use of COTS equipment designed for solidly grounded terrestrial applications
- Solidly ground system normally provided by:
 - Delta Wye transformer
 - 3 phase 208 volt line to line (120 volts line to neutral) secondary
 - Transformer Neutral Conductor solidly grounded
 - Single phase transformer connected line to line on primary
 - Secondary can be 120 volts with one conductor solidly grounded (neutral)
 - Secondary can be 240 volts with center tap solidly grounded (neutral)



Transformer Configurations

- Delta-Wye
 - 208 volts line to line
 - 120 volts line to ground
- Single Phase 240/120 Volt
 - Line to line on primary
 - Secondary center tap grounded.
- Single Phase 120 volt
 - One conductor grounded



Wye-Wye transformers are NOT recommended for solidly grounded secondary:

- With neutral of primary ungrounded, the current in neutral to ground connection of secondary is always zero.
- Line to ground fault on secondary results in
 - No current flows in the neutral of either transformer.
 - The neutral conductor on the secondary will have a voltage proportional to the faulted phase voltage.
 - The primary and secondary currents for the faulted phase will be in phase with the phase voltage.
 - The primary and secondary currents for the unfaulted phases will not be in phase with their respective phase voltages.
 - The fault current is limited by the load resistance



Simulation: Line to Ground Fault on Wye-Wye



20240504 wye-wye 3

Line to Ground Fault: Wye-Wye Secondary Voltages



Line to Ground Fault: Wye-Wye Primary Voltages







Line to Ground Fault: Wye-Wye Secondary Neutral Current



Line to Ground Fault: Delta-Wye



20240504 delta-wye 1

Line to Ground Fault: Delta-Wye Secondary Currents



Impact of unbalanced phase loads Delta-Wye Transformers

- Greater impact on secondary phase currents than on primary phase currents.
- Conductor current rating could be exceeded for one conductor on secondary while all conductors on primary are below their conductor current rating
- If unbalanced loads are possible, should provide circuit breakers on both primary and secondary side of transformer
 - Primary side protects transformer
 - Secondary side protects cable from transformer

Unbalanced Phase Loads



20240504 delta-wye 2

Unbalanced Phase Currents Secondary Phase Currents



Phase C current is twice the other phases



Phase A and C currents are about 150% of Phase B current

Grounding of panels and sub-panels



- IEEE 45.1-2023 Section 9.2
 - Ship structure should not be used as a normal current-carrying conductor for the electrical power supply distribution systems.
- System neutral should only be grounded at the Main Power Panel
 - Neutral is a current-carrying conductor
- Sub panels should not ground the system neutral.
 - Doing so will cause a portion of the neutral current to flow through the ship's structure
- Phase conductors, System neutral Conductor, and Equipment Ground Conductor (PE) should be part of the same cable
 - Maximize mutual inductance to minimize current through structure during a ground fault

Ground Fault on Neutral Conductor with NEMA 6-XX connectors

- Uses same conductor for neutral and equipment ground (PE) in terrestrial applications.
 - Commonly found on electric clothes dryers and kitchen stoves
- Important to use this conductor only for neutral in shipboard system.
 - Equipment ground (PE) provided by connection to hull.
 - Remove jumper from neutral to equipment chassis
 - Failure to remove jumper can result in large currents through the ship's hull.
- Instead, use NEMA 14-XX connectors with dedicated equipment ground (PE)





Simulation of grounded neutral on 208/120 volt system



20240504 delta-wye 3

Simulation of grounded neutral on 208/120 volt system: Currents



When Neutral is grounded at Load > .5 seconds, large structure current

Simulation of grounded neutral on 208/120 volt system: Voltages



Simulation of grounded neutral on 240/120 volt system



20240504 delta-wye 4

Simulation of grounded neutral on 240/120 volt system: Currents



When Neutral is grounded at Load > .5 seconds, large structure current

Simulation of grounded neutral on 240/120 volt system: Voltages



Ground Fault Detection

- Low impedance line to ground faults cleared by traditional circuit protection
- Low impedance neutral to ground faults are not cleared by traditional circuit protection
 - Can be detected by measuring current in transformer ground conductor
 - Can be cleared with GFCI
 - Not discussed in IEEE 45.1-2023
- High Impedance ground faults can be cleared with GFCI
- Traditional ground detection lamps should not be used on solidly grounded systems.

