



Bridge Rectifier should be rated at least 4 amps (5 or 6 is better) with a PIV rating greater than 100 Volts

Reversing Switch (used to establish which direction is forward for a given track polarity)

DC Tender Connections
 Norbert Doerry
 December 6, 2009